

P549 35 - 42, 48

$$(35) (a) C_{eq} = 6C = 6(4.7 \times 10^{-6} F) = \underline{28 \mu F}$$

$$(b) \frac{1}{C_{eq}} = \frac{6}{C} = \frac{6}{4.7 \times 10^{-6} F} \quad C_{eq} = \underline{0.78 \mu F}$$

(36) maximum (in parallel)

$$C_{eq} = 3200 \times 10^{-12} F + 7500 \times 10^{-12} F + 0.01 \times 10^{-6} F \\ = \underline{2.1 \times 10^{-8} F}$$

Minimum (in series)

$$C_{eq} = \left[ (3200 \times 10^{-12} F)^{-1} + (7500 \times 10^{-12} F)^{-1} + (0.01 \times 10^{-6} F)^{-1} \right]^{-1} \\ = \underline{1.8 \times 10^{-9} F}$$

$$(37) C_{series} = \left( \frac{1}{3 \times 10^{-6} F} + \frac{1}{4 \times 10^{-6} F} \right)^{-1} = 1.71 \times 10^{-6} F$$

$$C_{eq} = 2 \times 10^{-6} F + 1.71 \times 10^{-6} F = \underline{3.71 \times 10^{-6} F}$$

$$(38) V_{2\mu F} = \underline{26 V}$$

$$V_{series} = 26 V$$

$$C = \frac{q}{V}$$

$$q = CV = (1.71 \times 10^{-6} F)(26 V) \\ = 4.45 \times 10^{-5} C$$

$$V = \frac{q}{C}$$

$$V_{3\mu F} = \frac{4.45 \times 10^{-5} C}{3 \times 10^{-6} F} = \underline{15 V}$$

$$V_{4\mu F} = \frac{4.45 \times 10^{-5} C}{4 \times 10^{-6} F} = \underline{11 V}$$

- (39) To decrease capacitance, a capacitor must be added in series. This means existing connections must be broken.

$$C_{eq} = \left( \frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$$

$$C_2 = \left( \frac{1}{C_{eq}} - \frac{1}{C_1} \right)^{-1} = \left( \frac{1}{2900 \times 10^{-12} \text{ F}} - \frac{1}{4800 \times 10^{-12} \text{ F}} \right)^{-1}$$

$$\underline{C_2 = 7300 \text{ pF}}$$

- (40) An 11  $\mu\text{F}$  capacitor must be added in parallel.


$$(41) C_{2/3} = \left( \frac{1}{C_2} + \frac{1}{C_3} \right)^{-1}$$

$$C_{eq} = C_1 + \left( \frac{1}{C_2} + \frac{1}{C_3} \right)^{-1} = C_1 + \frac{C_2 C_3}{C_2 + C_3} = C_1 + \frac{C_2 C_3}{C_2 + C_3} = \frac{C_1 C_2 + C_1 C_3 + C_2 C_3}{C_2 + C_3}$$

$$(42) V_1 = 45 \text{ V} \quad q_1 = C_1 V_1 = (22.6 \times 10^{-6} \text{ F})(45 \text{ V}) = \underline{1.0 \times 10^{-3} \text{ C}}$$

$$V_{2/3} = 45 \text{ V} \quad q_{2/3} = C_{2/3} V_{2/3} = (60.27 \times 10^{-6} \text{ F})(45) = \underline{2.7 \times 10^{-3} \text{ C}} = q_2 = q_3$$

(48)

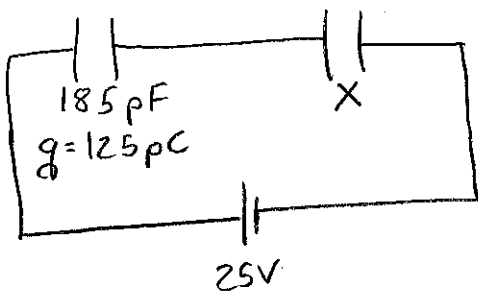

Since they are in series, both have the same charge and the equivalent capacitor also has the same charge.

$$C_{eq} = \frac{q}{V} = \frac{125 \times 10^{-12} \text{ C}}{25 \text{ V}} = 5 \times 10^{-12} \text{ F}$$

$$\frac{1}{C_{eq}} = \frac{1}{185 \times 10^{-12} \text{ F}} + \frac{1}{X}$$

$$X = \left( \frac{1}{C_{eq}} - \frac{1}{185 \times 10^{-12} \text{ F}} \right)^{-1} = \left( \frac{1}{5 \times 10^{-12} \text{ F}} - \frac{1}{185 \times 10^{-12} \text{ F}} \right)^{-1} = \underline{5.14 \times 10^{-12} \text{ F}}$$