

P612 30-38, 73, 74, 76, 79, 83

$$\textcircled{30} \quad \frac{V_p}{V_s} = \frac{N_p}{N_s}$$
$$N_s = \frac{N_p V_s}{V_p} = \frac{164(10000V)}{120V} = \underline{14000}$$

$$\textcircled{31} \quad \frac{N_p}{N_s} = \frac{V_p}{V_s}$$
$$\frac{320}{120} = \frac{V_p}{V_s} \quad \underline{V_s = 0.38 V_p} \quad \underline{\text{step-down}}$$

$$\frac{N_p}{N_s} = \frac{I_s}{I_p}$$
$$\frac{320}{120} = \frac{I_s}{I_p} \quad \underline{I_s = 2.7 I_p}$$

$$\textcircled{32} \quad \frac{V_p}{V_s} = \frac{I_s}{I_p}$$
$$\frac{25V}{120V} = \frac{I_s}{I_p} \quad \underline{I_s = 4.8 I_p}$$

$$\textcircled{33} \quad \frac{V_p}{V_s} = \frac{N_p}{N_s}$$
$$\frac{240V}{12000V} = \frac{N_p}{N_s} \quad \underline{\frac{N_s}{N_p} = 50}$$

If connected backwards

$$\frac{N_s}{N_p} = \frac{V_s}{V_p}$$
$$50 = \frac{240V}{V_p} \quad \underline{V_p = 4.8V}$$

$$(34) \quad (a) \quad \frac{V_p}{V_s} = \frac{I_s}{I_p}$$

$$V_s = \frac{V_p I_p}{I_s} = \frac{(120V)(0.35A)}{(7.5A)} = \underline{5.6V}$$

(b) step down

$$(35) \quad P = I V$$

$$I = \frac{P}{V} = \frac{95W}{12V} = 7.917A$$

$$\frac{V_p}{V_s} = \frac{I_s}{I_p}$$

$$V_s = \frac{I_p V_p}{I_s}$$

$$V_s = \frac{22A V_p}{7.917A}$$

$$(b) \quad V_s = 2.8 V_p \quad (a) \text{ step up}$$

$$(36) \quad \frac{V_p}{V_s} = \frac{N_p}{N_s}$$

$$V_s = \frac{N_s V_p}{N_p} = \frac{(1340)(120V)}{330} = \underline{490V}$$

$$\frac{I_p}{I_s} = \frac{N_s}{N_p}$$

$$I_p = \frac{N_s I_s}{N_p} = \frac{(1340)(15.0A)}{330} = \underline{61A}$$

Generator	4 Ω	Destination
? W		30 MW
? V		45 kV

(a) current is constant

$$P = IV$$

$$I = \frac{P}{V} = \frac{30 \times 10^6 \text{ W}}{45 \times 10^3 \text{ V}} = 667 \text{ A}$$

we lose emf (voltage) from transmission (voltage drop across a resistor)

$$V = IR$$

$$= (667 \text{ A})(4 \Omega) = 2668 \text{ V}$$

so the generation must have an emf of

$$45 \times 10^3 \text{ V} + 2668 \text{ V} = \underline{48 \text{ kV}}$$

(b) power dissipated (lost) in the transmission line

$$P = I^2 R = (667 \text{ A})^2 (4 \Omega) = 1.8 \times 10^6 \text{ W}$$

$$\frac{1.8 \times 10^6 \text{ W}}{30 \times 10^6 \text{ W}} = \underline{0.06 \text{ W lost}}$$

38) transmitting at 120 V

$$P = IV$$

$$I = \frac{P}{V} = \frac{65 \times 10^3 \text{ W}}{120 \text{ V}} = 542 \text{ A}$$

Power loss

$$P = I^2 R = (542 \text{ A})^2 (0.2 \Omega) = 5.88 \times 10^4 \text{ W}$$

stepping up and stepping down

$$P_1 \text{ --- } \Sigma P_2 \text{ --- } P_3 \text{ --- } \Sigma P_4$$

step up

$$P_2 = .99 P_1$$

$$P_2 = .99 (65 \times 10^3 \text{ W}) = 64350 \text{ W}$$

Transmission current

$$P = IV$$

$$I = \frac{P}{V} = \frac{64350 \text{ W}}{1200} = 53.6 \text{ A}$$

Power loss

$$P = I^2 R = (53.6 \text{ A})^2 (0.2 \Omega) = 574.6 \text{ W}$$

$$P_3 = P_2 - P_{\text{loss}} = 64350 - 575 = 63775 \text{ W}$$

step down

$$P_4 = .99 P_3 = .99 (63775 \text{ W}) = 63137 \text{ W}$$

Overall power loss

$$65 \times 10^3 \text{ W} - 63137 \text{ W} = 1863 \text{ W}$$

$$\text{Power Saved.} = 5.88 \times 10^4 \text{ W} - 1863 \text{ W} = \underline{5.7 \times 10^4 \text{ W}}$$

$$(73) \quad \mathcal{E} = -N \frac{d\Phi}{dt} = \frac{-NBA \cos\theta}{\Delta t} = \frac{-(.665T)(.24m)^2}{40 \times 10^{-3}s} = 0.958V$$

$$\text{Power} = \frac{\text{Energy}}{\Delta t}$$

$$P = \frac{V^2}{R} = \frac{(.958V)^2}{5.2\Omega} = 0.176W$$

$$\text{Energy} = P \Delta t = (0.176W)(40 \times 10^{-3}s) = \underline{7.04 \times 10^{-3} J}$$

(74) (a) step down

$$(b) P = IV$$

$$I = \frac{P}{V} = \frac{45W}{12V} = \underline{3.8A}$$

$$(c) \frac{I_s}{I_p} = \frac{V_p}{V_s}$$

$$I_p = \frac{V_s I_s}{V_p} = \frac{(12V)(3.8A)}{(120V)} = \underline{0.38A}$$

$$(d) P = I^2 R$$

$$R = \frac{P}{I^2} = \frac{45W}{(3.8A)^2} = \underline{3.1\Omega}$$

or

$$V = IR$$

$$R = \frac{V}{I} = \frac{12V}{3.8A} = 3.1\Omega$$

or

$$P = \frac{V^2}{R}$$

$$R = \frac{V^2}{P} = \frac{12V^2}{45W} = 3.2\Omega$$

76

(a) $P_s = .80 P_p$

$$P_p = \frac{P_s}{.8} = \frac{75W}{.8} = 93.75W$$

$$P = IV$$

$$I = \frac{P}{V} = \frac{93.75W}{110V} = 0.85 A$$


(b) current on secondary side

$$P = I^2 R$$

$$I = \sqrt{\frac{P}{R}} = \sqrt{\frac{75W}{2.4\Omega}} = 5.59 A$$

$$\frac{N_p}{N_s} = \frac{I_s}{I_p} = \frac{5.59 A}{0.85 A} = \underline{6.6}$$

79

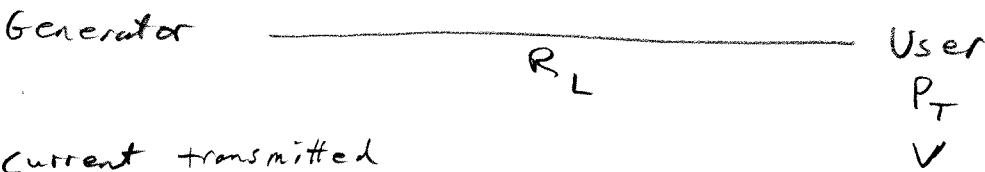

current transmitted

$$I = \frac{P}{V} = \frac{P_T}{V}$$

power loss

$$P = I^2 R$$

$$P_L = \frac{P_T^2 R_L}{V}$$

83 $V_o = 2\pi f N A B = 2\pi (120 \text{ Hz}) (155) (.066 \text{ m})^2 (0.2 \text{ T})$
 $= \underline{16.2 \text{ V}}$