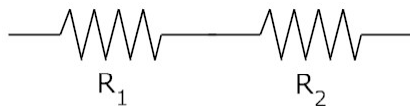


## Resistors in Series and in Parallel

### Series



- Voltage drop is different across each resistor
- The total voltage drop across the circuit is equal to the sum of the voltage drops across the individual resistors
- Current is the same through each resistor

## Series (math)


$$V_{eq} = V_1 + V_2$$

$$I_{eq}R_{eq} = I_1R_1 + I_2R_2$$

But...  $I_{eq} = I_1 = I_2$

Therefore...  $R_{eq} = R_1 + R_2$

## Parallel

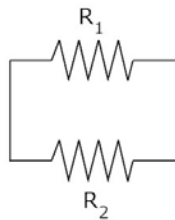

- Voltage drop across each resistor is the same
- Current through each resistor is different
- Total current through the circuit is the sum of the currents through each individual resistor

## Parallel (math)

$$I_{eq} = I_1 + I_2$$

$$\frac{V_{eq}}{R_{eq}} = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$


But...  $V_{eq} = V_1 = V_2$

Therefore... 
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

## Other Information

- A circuit with resistors in series is known as a **voltage divider**.
  - The voltage is divided among the resistors.
- A circuit with resistors in parallel is known as a **current divider**.
  - The current is divided among the resistors.

# Solving Circuits

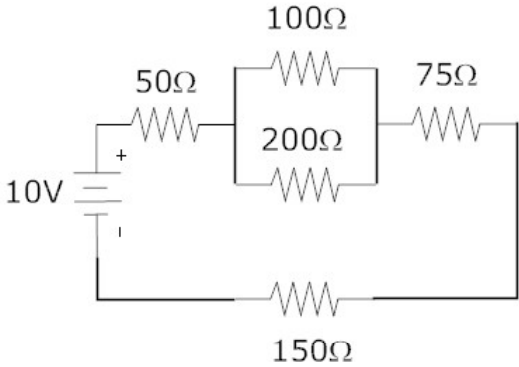

Calculate the equivalent resistance of the circuit, the voltage drop across each resistor, and the current through each resistor.


The  $100\ \Omega$  and the  $200\ \Omega$  resistors are in parallel

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{100\ \Omega} + \frac{1}{200\ \Omega}$$

$$\frac{1}{R_{eq}} = .015$$


$$R_{eq} = 67\ \Omega$$

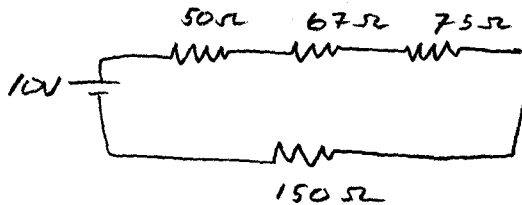

The  $50\ \Omega$ ,  $67\ \Omega$ ,  $75\ \Omega$  and  $150\ \Omega$  are in series


$$R_{eq} = 50\ \Omega + 67\ \Omega + 75\ \Omega + 150\ \Omega$$
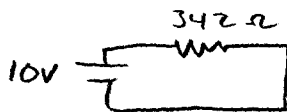
$$R_{eq} = 342\ \Omega \leftarrow \text{The equivalent resistance of the circuit}$$



$$V = IR$$
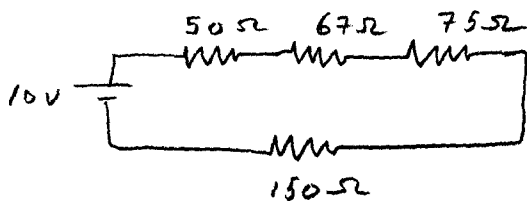
$$I = \frac{V}{R} = \frac{10V}{342\ \Omega} = 0.029\ A$$



Resistors are in series.

The same current flows through all resistors.

$$I_{50\ \Omega} = 0.029\ A$$

$$V_{50\ \Omega} = I_{50\ \Omega} R_{50\ \Omega} = (0.029\ A)(50\ \Omega) = \underline{1.45\ V}$$

$$I_{67\ \Omega} = 0.029\ A$$

$$V_{67\ \Omega} = (0.029\ A)(67\ \Omega) = 1.94\ V$$


$$I_{75\ \Omega} = 0.029\ A$$

$$V_{75\ \Omega} = (0.029\ A)(75\ \Omega) = \underline{2.18\ V}$$

$$I_{150\ \Omega} = 0.029\ A$$

$$V_{150\ \Omega} = (0.029\ A)(150\ \Omega) = \underline{4.35\ V}$$

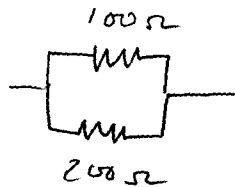The  $67\Omega$  is the equivalent resistance of 2 resistors in parallel



Resistors are in parallel.  
The voltage drop across each resistor is the same

$$\underline{V_{100\Omega} = 1.94V}$$

$$\underline{I_{100\Omega}} = \frac{V_{100\Omega}}{R_{100\Omega}} = \frac{1.94V}{100\Omega} = \underline{0.019A}$$

$$\underline{V_{200\Omega} = 1.94V}$$

$$\underline{I_{200\Omega}} = \frac{1.94V}{200\Omega} = \underline{0.010A}$$