
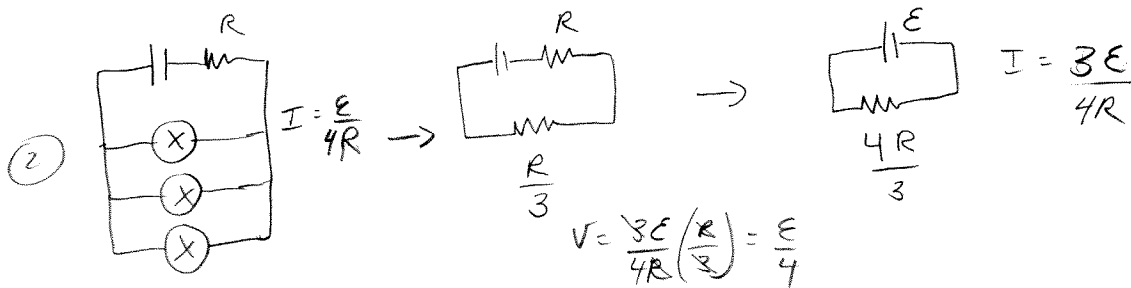


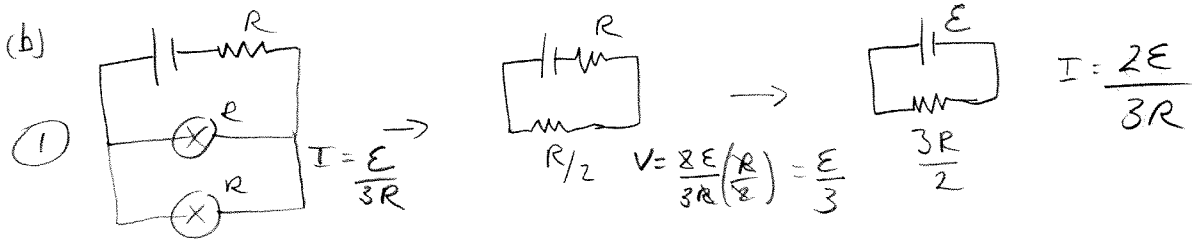- 29 (a) - bulbs are in parallel and therefore have the same voltage drop across them, \mathcal{E}
 - bulbs are identical and so they pull the same current
 \therefore the brightness will be the same



$$\frac{P_1}{P_2} = \frac{I_1^2 R_1}{I_2^2 R_2} = \frac{\left(\frac{\mathcal{E}}{3R} \right)^2 R}{\left(\frac{\mathcal{E}}{4R} \right)^2 R} = \frac{1}{9} = \frac{16}{9} \text{ times brighter}$$

30 $V_D = 8V$ $V_R = 12V - 8V = 4V$
 $I_D = 2A$ $I_R = 2A$ (resistors are in series)

$$R = \frac{V}{I} = \frac{4V}{2A} = \underline{2\Omega}$$

31 (a) P (only one device in the circuit)

(b) $2P$ (two devices in parallel - same \mathcal{E} , same I - so both dissipate P)

(c) $\frac{P}{2}$ (two devices in series)

(d) $R_{eq} = \left(\frac{1}{2R} + \frac{1}{R} \right)^{-1} = \frac{3R}{2}$ so power dissipated would be $\frac{3}{2}P$

32) an ideal voltmeter has $R = \infty \Omega$
 so all of voltage would be dropped across the voltmeter
12V

33) same reasoning as 32
6V

34) (a) Internal resistance = slope = $-\frac{\Delta V}{\Delta I} = -\frac{(2.4 - 8)}{(1.8 - 3.2)} = \underline{1.2 \Omega}$


(b) $V = Ir = (3.2 A)(1.2 \Omega) = 3.84V$ across the internal resistor.
 8V across battery

$\therefore \mathcal{E} = 8V + 3.84V = \underline{12V}$

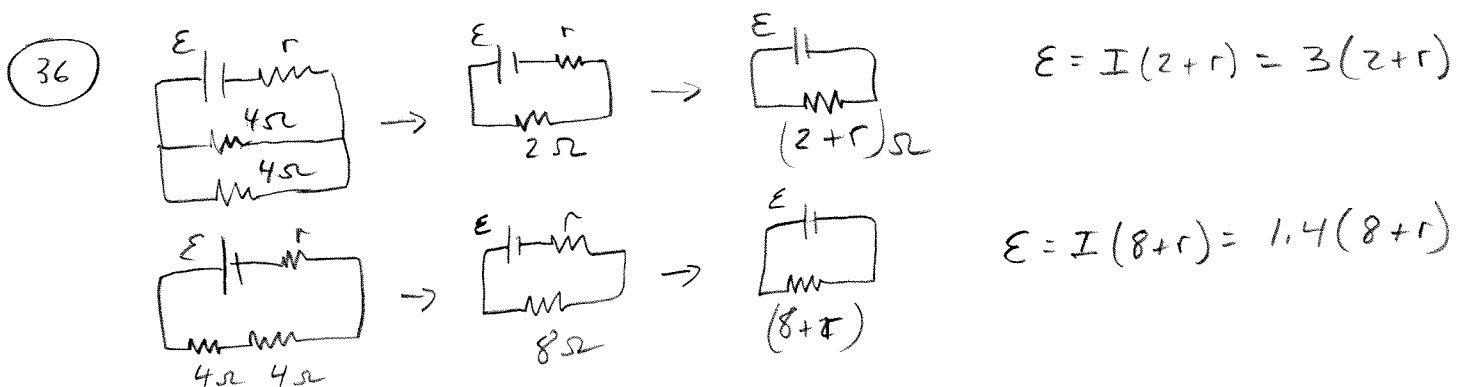35) $\frac{I}{R} = \frac{V}{R} = \frac{1.2V}{1.5\Omega} = 0.8A$

from graph $0.8A \rightarrow 1.6V$

$\therefore \text{EMF} = 1.2V + 1.6V = \underline{2.8V}$



(b)

$$3(2+r) = 1.4(8+r)$$

$$6 + 3r = 11.2 + 1.4r$$


$$1.6r = 5.2$$

$$r = \underline{3.25\Omega}$$

(a) $\mathcal{E} = 3(2+r)$
 $= 3(2 + 3.25)$
 $= \underline{16V}$

37

(a)

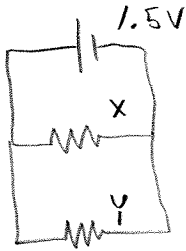


from graph (1.5V)

$$I_x = 2.67 \text{ A}$$

$$I_y = 1.53 \text{ A}$$

$$\text{Total Current} = I_x + I_y = 2.67 \text{ A} + 1.53 \text{ A} = \underline{4.2 \text{ A}}$$

(b)

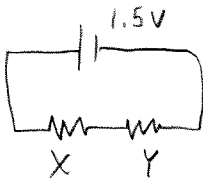

$$V_x + V_y = 1.5 \text{ V}$$

$$I_x = I_y$$

using the graph, find a current that gives two voltages that add to 1.5V

$$I = 1.1 \text{ A} \quad (V_x = 0.6 \text{ V}, V_y = 1.0 \text{ V})$$

38

- voltage will not change (parallel circuit)
- PTC R increases, so I decreases
- NTC R decreases, so I increases

A will be dimmer, B will be brighter

39

(a) 39Ω (from graph)

$$(b) R_{eq} = R_{NTC} + 25$$

$$I = \frac{V}{R} = \frac{9.0 \text{ V}}{R_{NTC} + 25}$$

Voltmeter is measuring voltage drop across R_{NTC} .

$$V = IR = \frac{9.0(R_{NTC})}{R_{NTC} + 25}$$

$$(c) V = \frac{9.0(39 \Omega)}{39 \Omega + 25} = \underline{5.5 \text{ V}}$$

- (d) - Voltmeter reading can be calibrated for temperature.
 - as temperature changes, the voltage will change.

(40) (a) 4.0V

(b) $R = \frac{V}{I} = \frac{4V}{0.2A} = 20\Omega$

(c) $R_{eq} = \left(\frac{1}{60} + \frac{1}{20}\right)^{-1} = 15\Omega + 60\Omega = \underline{75\Omega}$
Total R

$I = \frac{V}{R} = \frac{8V}{75\Omega} = 0.107A$

$V = IR = (0.107A)(15\Omega) = \underline{1.6V}$

(d) $I = \frac{V}{R} = \frac{1.6V}{20\Omega} = \underline{0.08A}$

(e) there is not enough current to light the bulb.

(41) (a) $R_{eq} = \left(\frac{1}{100\Omega} + \frac{1}{100\Omega}\right)^{-1} = 50\Omega + 100\Omega = 150\Omega$

$I = \frac{V}{R} = \frac{6V}{150\Omega} = 0.04A$

$V = IR = (0.04A)(50\Omega) = \underline{2V}$

(b) $R_{eq} = \left(\frac{1}{110\Omega} + \frac{1}{100\Omega}\right)^{-1} = 52.38 + 100\Omega = 152.38\Omega$

$I = \frac{V}{R} = \frac{6V}{152.38} = 0.039A$

$V = IR = (0.039A)(52.38) = \underline{2.06V}$