

$$\textcircled{1} R = \frac{\rho L}{A} \quad A = \pi r^2$$

$$R \propto \frac{1}{r^2}$$

$$\underline{.25}$$

$\textcircled{2}$ 12Ω (The resistance of the resistor does not depend on current).

$$\textcircled{3} R = \frac{\rho L}{A} \quad A = \pi r^2$$

$$R \propto \frac{1}{r^2} \quad r = .5$$


$$4R \quad \underline{R = 40.0 \Omega}$$

$$\textcircled{4} \text{ (a) } P = \frac{V^2}{R}$$

$$R = \frac{V^2}{P} = \frac{(220V)^2}{120W} = \underline{4.0 \times 10^2 \Omega} \quad (403 \Omega)$$

$$\text{ (b) } R = \frac{\rho L}{A} \quad A = \pi r^2$$
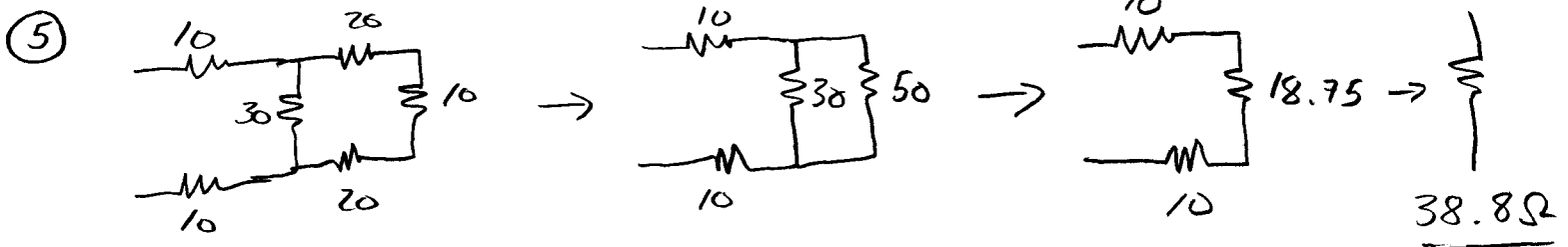
$$L = \frac{\pi r^2 R}{\rho} = \frac{\pi (0.03 \times 10^{-3} m)^2 (403 \Omega)}{2 \times 10^{-6} \Omega m} = \underline{0.57 m}$$




$$\textcircled{6} \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \quad R_1 = R_2 = \frac{R}{2}$$

$$= \frac{1}{\frac{R}{2}} + \frac{1}{\frac{R}{2}} = \frac{2}{R} + \frac{2}{R} = \frac{4}{R}$$

$$\underline{R_{eq} = \frac{R}{4}}$$


7

(a)

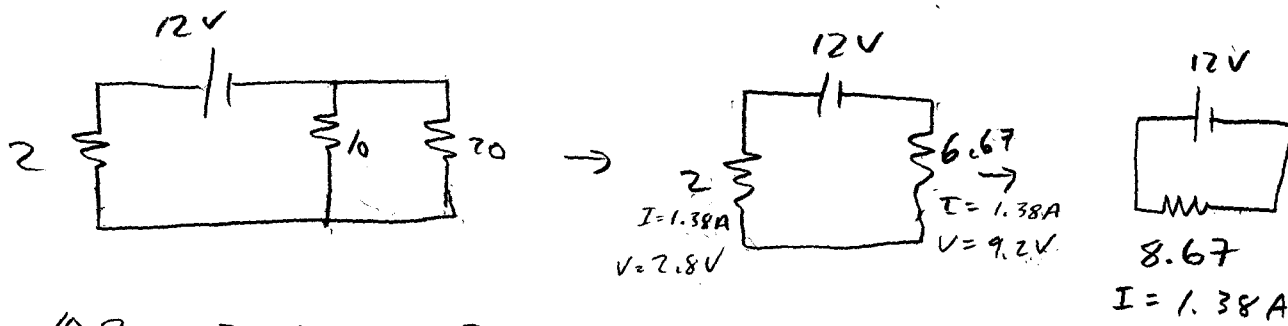


$\frac{10\Omega}{20\Omega}$	$\frac{20\Omega}{20\Omega}$	$\frac{2\Omega}{20\Omega}$
$V = 9.2V$	$9.2V$	$2.8V$
$I = 0.92A$	$0.46A$	$1.38A$

(b)

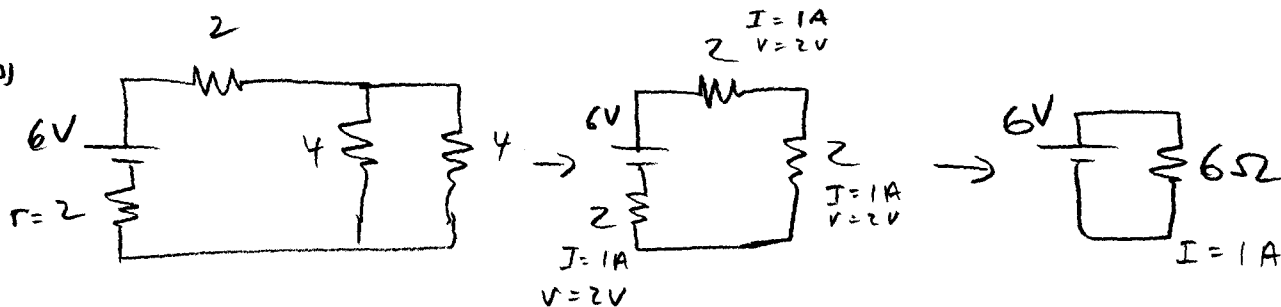

$\frac{4\Omega}{2\Omega}$	$\frac{2\Omega}{2\Omega}$
$V = 2V$	$2V$
$I = 0.5A$	$1A$

8

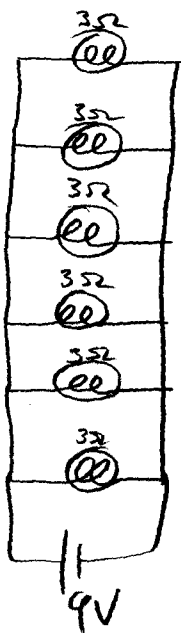

$$P = \frac{V^2}{R}$$

- since the bulbs are in parallel, the voltage drop will be the same (9V) across each light bulb
- all light bulbs have the same resistance so all bulbs will have the same power.
- if one bulb burns out, the remaining bulbs are still in parallel and therefore will still have a voltage drop of 9V, giving the same power.

∴ the brightness will be the same.

⑨ (a) Toaster: $P = IV$

$$I = \frac{P}{V} = \frac{1200 \text{ W}}{220 \text{ V}} = \underline{5.45 \text{ A}}$$

Mixer: $I = \frac{P}{V} = \frac{500 \text{ W}}{220 \text{ V}} = \underline{2.27 \text{ A}}$

(b) $E = Pt$

Toaster: $E = 1200 \text{ W} \times 1 \text{ h} = 1200 \text{ Wh} = \underline{1.2 \text{ kWh}}$

Mixer: $E = 500 \text{ W} \times 1 \text{ h} = 500 \text{ Wh} = \underline{0.5 \text{ kWh}}$

⑩ (a) $P = IV$

$$I = \frac{P}{V} = \frac{2000 \text{ W}}{220 \text{ V}} = \underline{9 \text{ A}}$$

(b) $P = \frac{V^2}{R}$

$$R = \frac{V^2}{P} = \frac{(220 \text{ V})^2}{2000 \text{ W}} = \underline{24 \Omega}$$

(c) $Q = mc\Delta T$

$$= (2 \text{ kg})(4200 \text{ J kg}^{-1} \text{ K}^{-1})(90 - 15^\circ \text{C})$$


$$= 6.3 \times 10^5 \text{ J}$$

$P = 2000 \text{ W} = 2000 \text{ J s}^{-1}$

$$\frac{6.3 \times 10^5 \text{ J}}{2000 \text{ J s}^{-1}} = 315 \text{ s} = \underline{5.25 \text{ min}} = 0.0875 \text{ h}$$

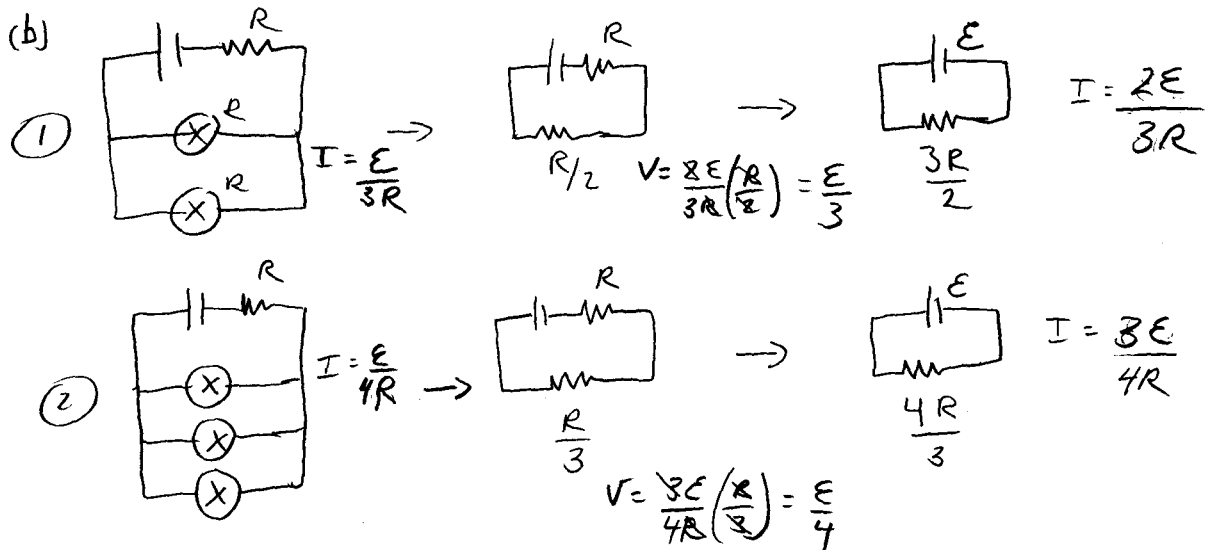(d) $2000 \text{ W} (.0875 \text{ h}) = 175 \text{ Wh} = 0.175 \text{ kWh} (\neq 0.10) = \underline{0.02}$

- 29 (a) - bulbs are in parallel and therefore have the same voltage drop across them, \mathcal{E}
 - bulbs are identical and so they pull the same current
 \therefore the brightness will be the same



$$\frac{P_1}{P_2} = \frac{I_1^2 R_1}{I_2^2 R_2} = \frac{\left(\frac{E}{3R}\right)^2 R}{\left(\frac{E}{4R}\right)^2 R} = \frac{1}{9} = \frac{16}{9} \text{ times brighter}$$

30 $V_D = 8V$ $V_R = 12V - 8V = 4V$
 $I_D = 2A$ $I_R = 2A$ (resistors are in series)

$$R = \frac{V}{I} = \frac{4V}{2A} = \underline{2\Omega}$$

31 (a) P (only one device in the circuit)

(b) $2P$ (two devices in parallel - same \mathcal{E} , same I - so both dissipate P)

(c) $\frac{P}{2}$ (two devices in series)

(d) $R_{eq} = \left(\frac{1}{2R} + \frac{1}{R}\right)^{-1} = \frac{3R}{2}$ so power dissipated would be $\frac{3}{2}P$

32) an ideal voltmeter has $R = \infty \Omega$
 so all of voltage would be dropped across the voltmeter
12V

33) same reasoning as 32
6V

34) (a) Internal resistance = slope = $-\frac{\Delta V}{\Delta I} = -\frac{(2.4 - 8)}{(18 - 3.2)} = \underline{1.2 \Omega}$


(b) $V = IR = (3.2 A)(1.2 \Omega) = 3.84V$ across the internal resistor.
 8V across battery

$\therefore \mathcal{E} = 8V + 3.84V = \underline{12V}$

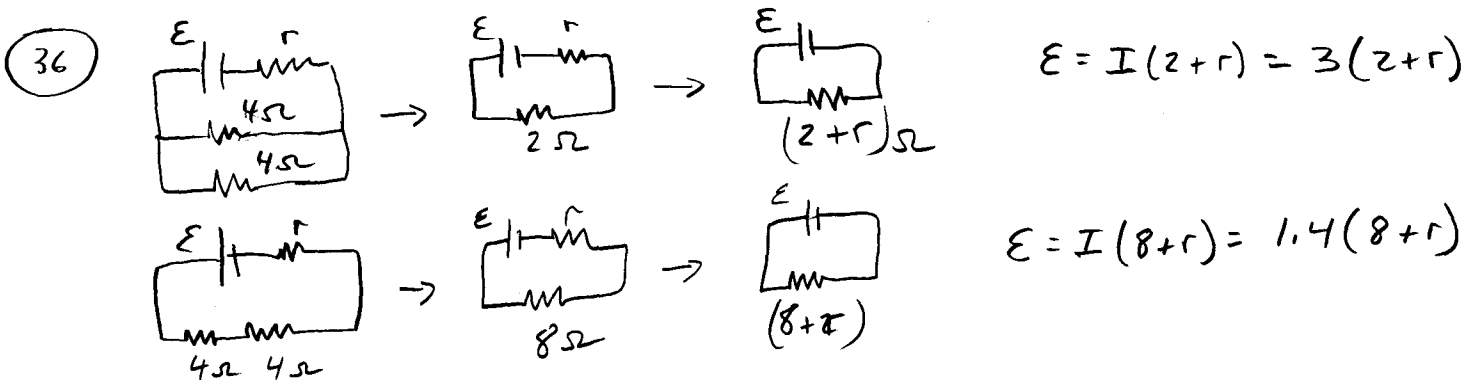35) $\frac{I}{R} = \frac{V}{R} = \frac{1.2V}{1.5\Omega} = 0.8A$

from graph $0.8V \rightarrow 1.6V$

$\therefore \text{EMF} = 1.2V + 1.6V = \underline{2.8V}$



(b)

$$3(2+r) = 1.4(8+r)$$

$$6 + 3r = 11.2 + 1.4r$$

$$1.6r = 5.2$$

$$r = \underline{3.25\Omega}$$


(a)

$$\mathcal{E} = 3(2+r)$$

$$= 3(2 + 3.25)$$

$$= \underline{16V}$$

37

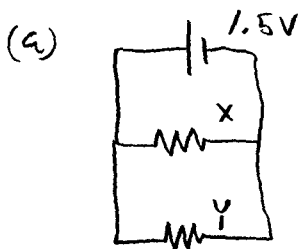


from graph (1.5V)

$$I_x = 2.67A$$

$$I_y = 1.53A$$
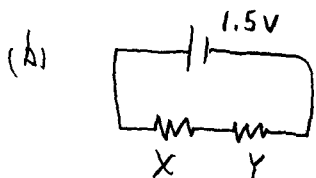
$$\text{Total Current} = I_x + I_y = 2.67A + 1.53A = \underline{4.2A}$$



$$V_x + V_y = 1.5V$$

$$I_x = I_y$$

using the graph, find a current that gives two voltages that add to 1.5V

$$I = 1.1A \quad (V_x = 0.6V, V_y = 1.0V)$$

38

- voltage will not change (parallel circuit)

- PTC R increases, so I decreases

- NTC R decreases, so I increases

A will be dimmer, B will be brighter

39

(a) 39Ω (from graph)

$$(b) R_{eq} = R_{NTC} + 25$$

$$I = \frac{V}{R} = \frac{9.0V}{R_{NTC} + 25}$$

Voltmeter is measuring voltage drop across R_{NTC} .

$$V = IR = \frac{9.0(R_{NTC})}{R_{NTC} + 25}$$

$$(c) V = \frac{9.0(39\Omega)}{39\Omega + 25} = \underline{5.5V}$$

(d) - Voltmeter reading can be calibrated for temperature.

- as temperature changes, the voltage will change.

(40) (a) 4.0V

(b) $R = \frac{V}{I} = \frac{4V}{0.2A} = 20\Omega$

(c) $R_{eq} = \left(\frac{1}{60} + \frac{1}{20}\right)^{-1} = 15\Omega + 60\Omega = 75\Omega$
Total R.

$I = \frac{V}{R} = \frac{8V}{75\Omega} = 0.107A$

$V = IR = (0.107A)(15\Omega) = \underline{1.6V}$

(d) $I = \frac{V}{R} = \frac{1.6V}{20\Omega} = \underline{0.08A}$

(e) there is not enough current to light the bulb.

(41) (a) $R_{eq} = \left(\frac{1}{100\Omega} + \frac{1}{100\Omega}\right)^{-1} = 50\Omega + 100\Omega = 150\Omega$

$I = \frac{V}{R} = \frac{6V}{150\Omega} = 0.04A$

$V = IR = (0.04A)(150\Omega) = \underline{2V}$

(b) $R_{eq} = \left(\frac{1}{110\Omega} + \frac{1}{100\Omega}\right)^{-1} = 52.38 + 100\Omega = 152.38\Omega$

$I = \frac{V}{R} = \frac{6V}{152.38} = 0.039A$

$V = IR = (0.039A)(52.38) = \underline{2.06V}$