

**B3.** This question is in **three** parts. **Part 1** is about electrical components. **Part 2** is about magnetic forces and **Part 3** is about electromagnetic induction.

**Part 1** Electrical components

(a) In the space below, draw a circuit diagram that could be used to determine the current-voltage ( $I$ - $V$ ) characteristics of an electrical component X. [2]




*(This question continues on the following page)*



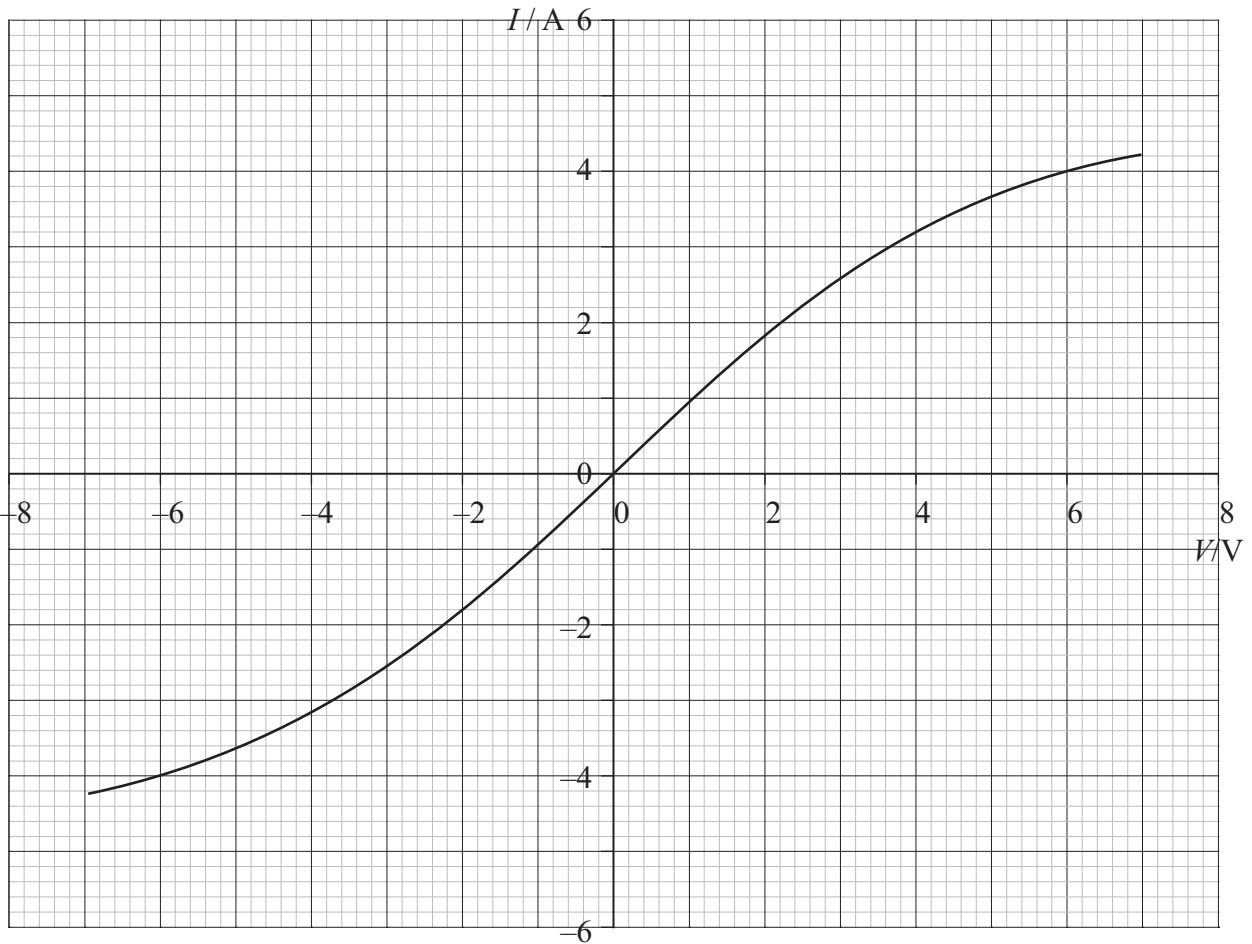(Question B3, part 1 continued)

The graph below shows the  $I$ - $V$  characteristics for the component X.



The component X is now connected across the terminals of a battery of e.m.f. 6.0 V and negligible internal resistance.

(b) Use the graph to determine

(i) the current in component X.

[1]

.....

(ii) the resistance of component X.

[2]


.....  
.....  
.....

(This question continues on the following page)



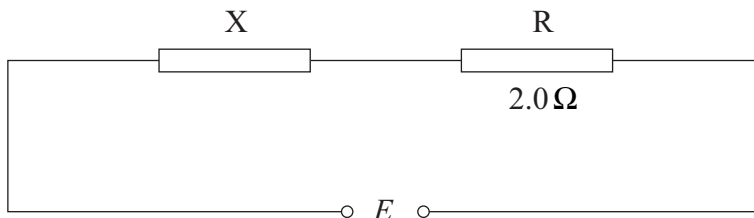(Question B3, part 1 continued)

A resistor R of constant resistance  $2.0\ \Omega$  is now connected in series with component X as shown below.



(c) (i) On the graph opposite, draw the  $I$ - $V$  characteristics for the resistor R. [2]

(ii) Determine the total potential difference  $E$  that must be applied across component X and across resistor R such that the current through X and R is 3.0 A. [2]

.....  
.....  
.....

(This question continues on the following page)

