

P 48 23 - 27, 32, 71

$$\textcircled{23} R_{\text{eq}} = 2.0\Omega + 12.0\Omega + 8.0\Omega = 22\Omega$$

$$I = \frac{V}{R} = \frac{9.0V}{22\Omega} = \underline{.41A}$$

$$\begin{aligned}\Sigma V &= 9.0V - (.41A)(8.0\Omega) - (.41A)(12.0\Omega) - (.41A)(2.0\Omega) \\ &= \underline{0}\end{aligned}$$

$$\textcircled{24} \Sigma V = 0$$

$$-18V - 1.0\Omega(I) - 2.0\Omega(I) + 12V - 6.6\Omega(I) = 0$$

$$-6V - 9.6\Omega(I) = 0$$

$$I = -.625A$$

$$\textcircled{P}_{18V}: V = (.625A)(1.0\Omega) = .625V \text{ drop across resistor}$$

$$\therefore \underline{V_{18} = 17.4V}$$

$$\textcircled{P}_{12V}: V = (.625A)(2.0\Omega) = 1.25V \text{ drop across resistor}$$

$$\therefore \underline{V_{12} = 10.8V}$$

$$\textcircled{25} (a) \Sigma V_{\text{top loop}} = -30I_1 + 45V - 1I_3 - 40I_3 = 0$$

$$-30I_1 - 41I_3 = 45$$

$$\Sigma V_{\text{outside loop}} = -30I_1 + 20I_2 + 1I_2 - 80V = 0$$

$$-30I_1 + 21I_2 = 80$$

$$I_a: I_3 = I_1 + I_2$$

to find the potential difference between a and d
we need to calculate I_3

$$25a \quad I_3 = \frac{-45 + 30I_1}{-41} = 1.10 - .73I_1$$

$$I_1 = \frac{80 - 21I_2}{-30} = -2.67 + .7I_2$$

$$I_3 = I_1 + I_2$$

$$1.10 - .73I_1 = I_1 + I_2$$

$$1.10 - .73(-2.67 + .7I_2) = (-2.67 + .7I_2) + I_2$$

$$1.10 + 1.949 - .511I_2 = -2.67 + 1.7I_2$$

$$5.719 = 2.211I_2$$

$$I_2 = 2.59 \text{ A}$$

$$I_1 = -2.67 + .7(2.59)$$

$$I_1 = -0.857 \text{ A}$$

$$I_3 = I_1 + I_2 = -0.857 + 2.59$$

$$= 1.733 \text{ A}$$

$$V_{ad} = 45 - 1I_3 - 40I_3 = 45 - 41(1.733) = \underline{-26 \text{ V}}$$

$$(b) \quad V_{80} = 80V - 1I_2 = 80 - (2.59) = \underline{77 \text{ V}}$$

$$V_{45} = 45V - 1I_3 = 45 - (1.733) = \underline{43 \text{ V}}$$

$$\textcircled{26} \sum V_{\text{loop}} = -IR - 1.5V - IR - IR - 1.5V - IR = 0$$

$$-4IR = 3$$

$$I = \frac{3}{-4R} = \frac{3}{-4(75)} = -0.01 \text{ A}$$


$$V_{ab} = -IR - 1.5V - IR$$

$$= -2IR - 1.5V = -2(-0.01 \text{ A})(75 \Omega) - 1.5V = \underline{0}$$

$$\textcircled{27} \sum V_{\text{top}} = -9.0V + 22I_1 + 15I_3 = 0$$

$$\sum V_{\text{bottom}} = -15I_3 - 6V = 0$$

$$I_a: I_2 = I_1 + I_3$$

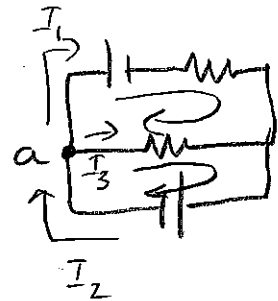

$$I_3 = \frac{6}{-15} = -0.4 \text{ A}$$

$$-22I_1 = 9 - 15I_3$$

$$I_1 = \frac{9 - 15I_3}{-22} = \frac{9 - 15(-0.4)}{-22} = -0.68$$

I_{R_1} 0.68 A right to left

I_{R_2} 0.40 A right to left

$$\textcircled{32} \text{ (a) } \sum V_{\text{top loop}} = 1I_1 - 12 + 12I_1 + 10I_2 + 1I_2 - 12 + 8I_1 = 0$$
$$21I_1 + 11I_2 = 24$$

$$\sum V_{\text{bottom loop}} = 12 - 1I_2 - 10I_2 + 18I_3 + 1I_3 - 6 + 15I_3 = 0$$
$$-11I_2 + 34I_3 = -6$$

$$I_{\text{left junction}}: I_1 = I_2 + I_3$$

$$I_1 = \frac{24 - 11I_2}{21} = 1.14 - .523I_2$$

$$I_3 = \frac{-6 + 11I_2}{34} = -.176 + .324I_2$$

$$(1.14 - .523I_2) = I_2 + (-.176 + .324I_2)$$


$$1.316 = 1.847I_2$$

$$\underline{I_2 = 0.71 \text{ A}}$$

$$I_1 = 1.14 - .523(.71) = \underline{0.77 \text{ A}}$$

$$I_3 = -.176 + .324(.71) = \underline{0.054 \text{ A}}$$

71 (a)

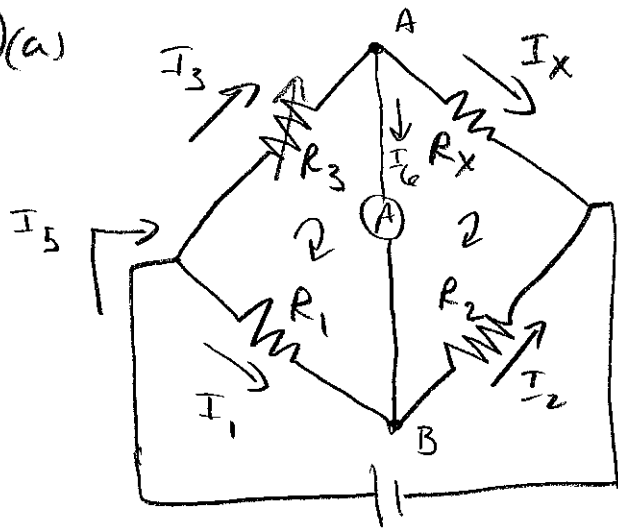

$$\sum V_{\text{left}} = -I_3 R_3 + I_1 R_1 = 0$$

$$\sum V_{\text{right}} = -I_x R_x + I_2 R_2 = 0$$

$$I_A: I_3 = I_6 + I_x$$

$$I_B: I_1 + I_6 = I_2$$

But $I_6 = 0$ if the bridge is balanced.

$$\text{So... } I_3 = I_x$$

$$I_1 = I_2$$

$$I_x R_x = I_2 R_2$$

$$R_x = \frac{I_2 R_2}{I_x}$$

$$\underline{R_x = \frac{R_2 R_3}{R_1}}$$

$$I_3 R_3 = I_1 R_1$$

$$I_x R_3 = I_2 R_1$$

$$I_x = \frac{I_2 R_1}{R_3}$$

$$(b) R_x = \frac{(972 \Omega)(42.6 \Omega)}{630 \Omega} = \underline{65.7 \Omega}$$