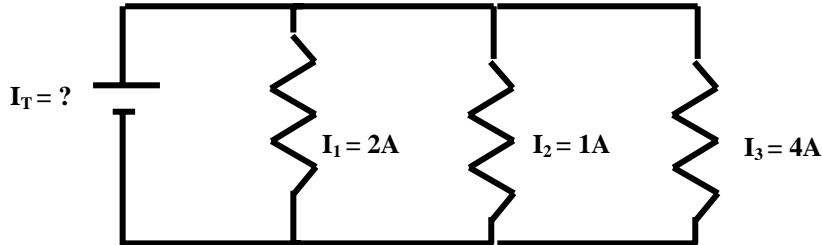



CIRCUIT MATH

Solve the following problems showing all work.

1. Find I_T for the following circuit.




2. Complete the table for this circuit.

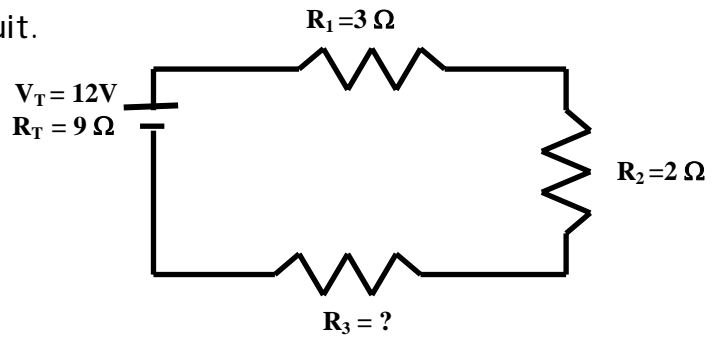


$V_T = 12 \text{ V}$	$V_1 =$	$V_2 =$	$V_3 =$
$R_T = 9 \Omega$	$R_1 = 3 \Omega$	$R_2 = 2 \Omega$	$R_3 =$
$I_T =$	$I_1 =$	$I_2 =$	$I_3 =$

3. Complete the table for this circuit.

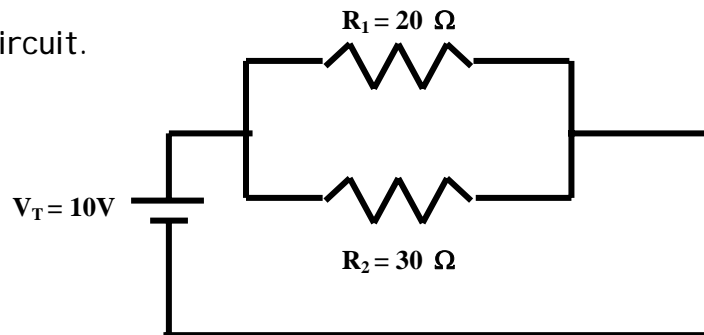

$V_T = 10 \text{ V}$	$V_1 =$	$V_2 =$
$R_T =$	$R_1 = 20 \Omega$	$R_2 = 30 \Omega$
$I_T =$	$I_1 =$	$I_2 =$

4. Find the following.

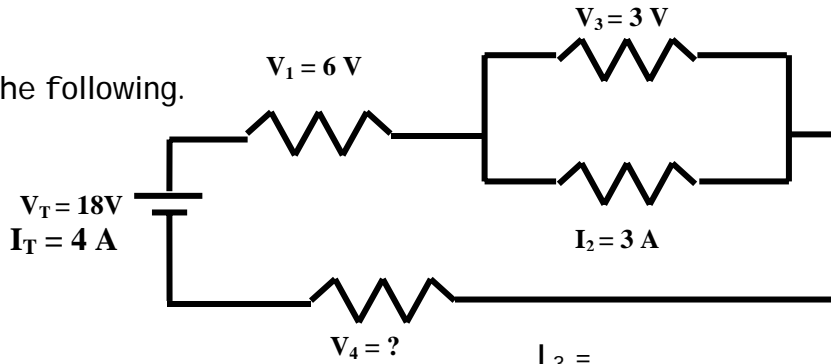


$V_2 = \underline{\hspace{2cm}}$

$I_3 = \underline{\hspace{2cm}}$

$V_4 = \underline{\hspace{2cm}}$

$I_4 = \underline{\hspace{2cm}}$

5. Find the following.

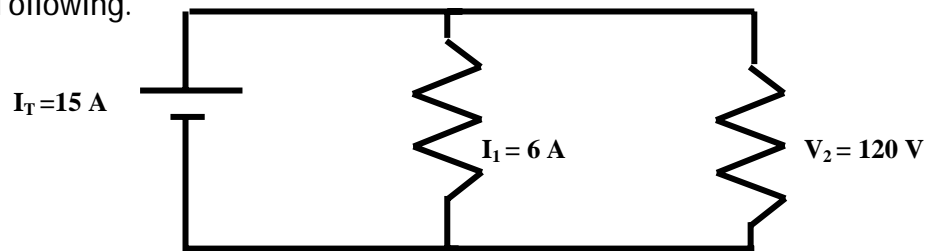

$V_T = \underline{\hspace{2cm}}$


$R_1 = \underline{\hspace{2cm}}$

$V_1 = \underline{\hspace{2cm}}$

$R_2 = \underline{\hspace{2cm}}$

$I_2 = \underline{\hspace{2cm}}$

6. Find the following.

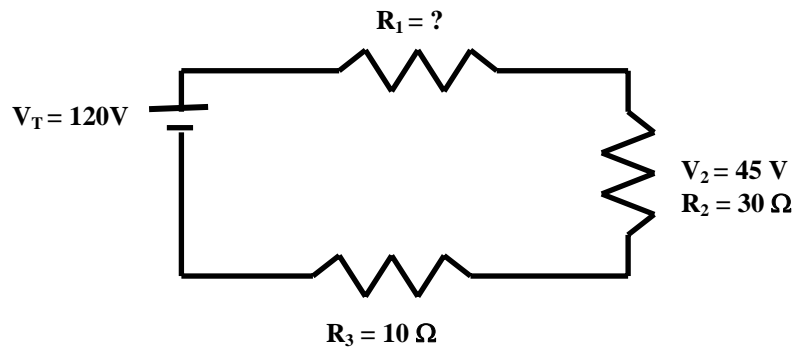

$V_3 = \underline{\hspace{2cm}}$

$I_3 = \underline{\hspace{2cm}}$

$V_1 = \underline{\hspace{2cm}}$


$R_1 = \underline{\hspace{2cm}}$

$I_1 = \underline{\hspace{2cm}}$

$R_T = \underline{\hspace{2cm}}$

$I_2 = \underline{\hspace{2cm}}$

7. Find the following.

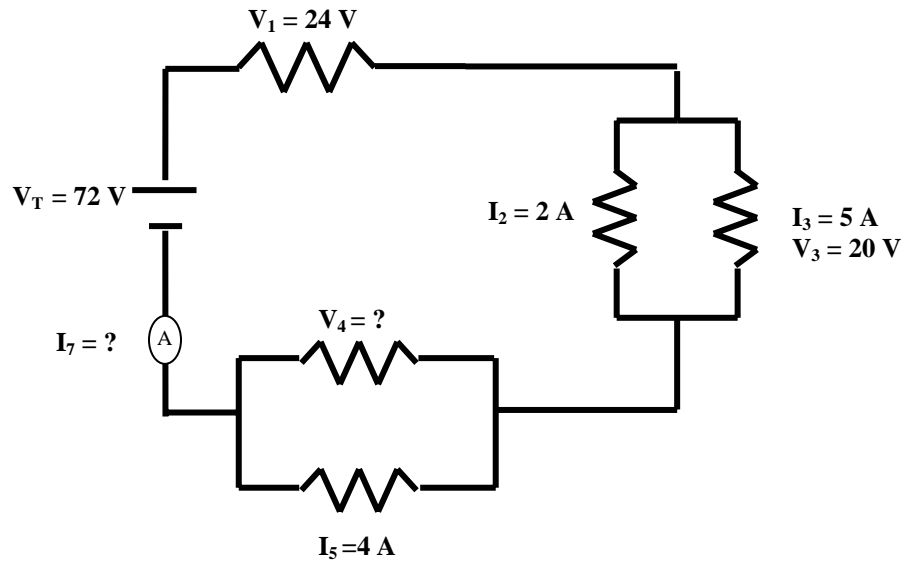

$I_1 = \underline{\hspace{2cm}}$

$V_5 = \underline{\hspace{2cm}}$

$V_2 = \underline{\hspace{2cm}}$

$I_4 = \underline{\hspace{2cm}}$

$V_4 = \underline{\hspace{2cm}}$

$I_7 = \underline{\hspace{2cm}}$