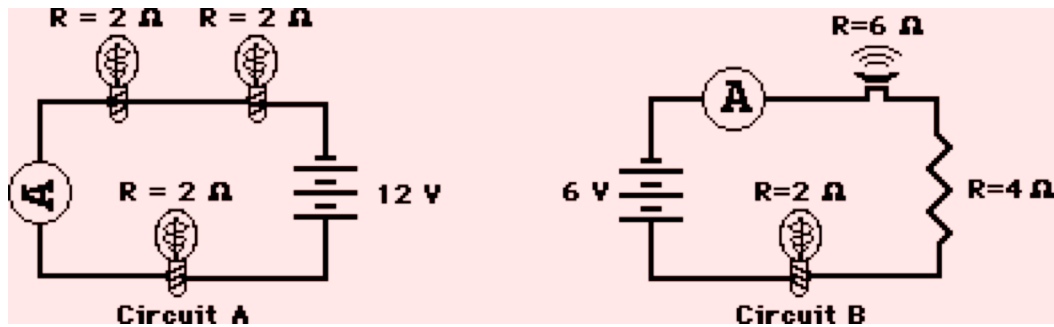


7. Analyze the following circuit and determine the equivalent or total resistance. Then determine the current at the ammeter location.





$R_{tot} =$  \_\_\_\_\_

$I =$  \_\_\_\_\_

$R_{tot} =$  \_\_\_\_\_


$I =$  \_\_\_\_\_

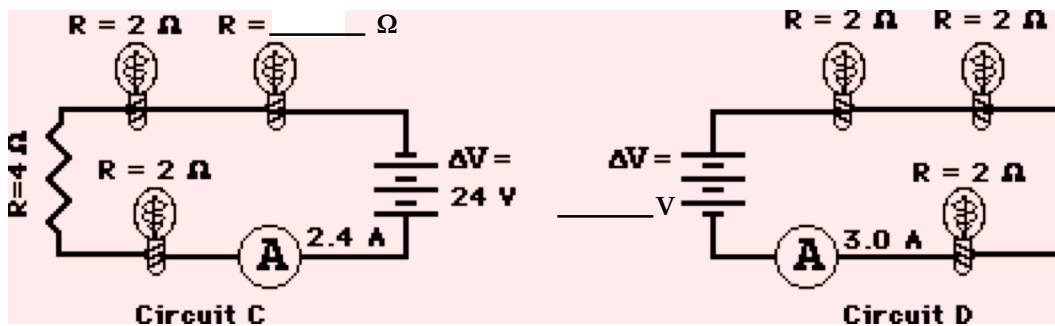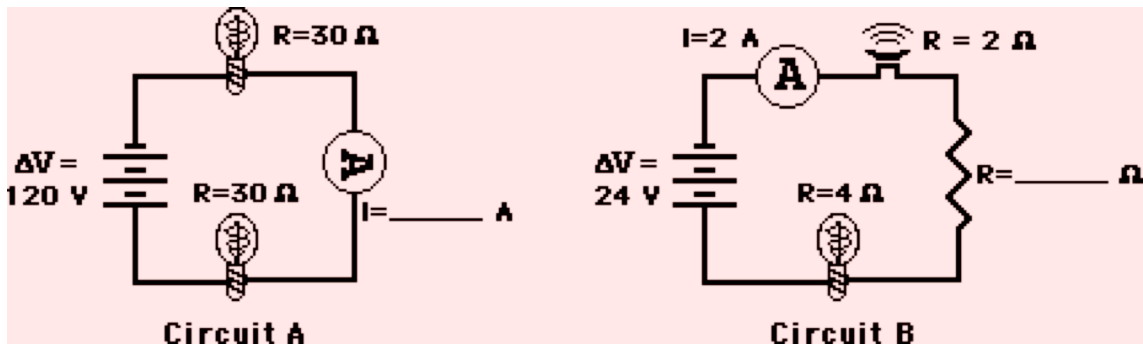8. For the following diagrams, utilize the concept of equivalent resistance and Ohm's Law in order to fill in the blank.




## Electric Circuits

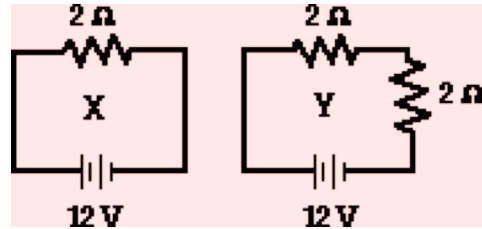
9. Compare circuits X and Y. Consider circuits X and Y below. Each circuit is powered by the same battery and contains identical resistors. Circuit X has one resistor and circuit Y has two resistors. The equivalent resistance of circuit X will be \_\_\_\_\_ ( $>$  or  $<$  or  $=$ ) that of circuit Y. The current in the battery in X will be \_\_\_\_\_ ( $>$  or  $<$  or  $=$ ) that in the battery in Y.



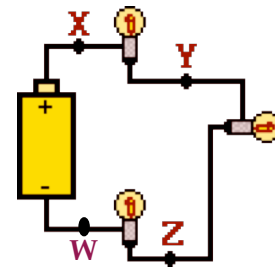10. Three identical light bulbs are connected to a battery as shown below. Which adjustments could be made to the circuit that would increase the current being measured at X? Circle all that apply.
- Increase the resistance of one of the bulbs.
  - Decrease the resistance of two of the bulbs.
  - Increase the resistance of two of the bulbs.
  - Decrease the voltage of the battery.
  - Increase the voltage of the battery.
  - Remove one of the bulbs (and re-connect the circuit).




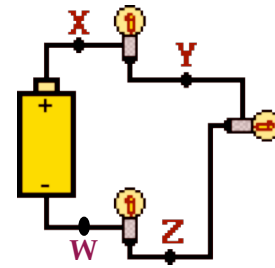11. Three identical light bulbs are connected to a battery as shown below. W, X, Y and Z represent locations along the circuit. Which one of the following statements is true?
- The potential difference between X and Y is greater than that between Y and Z.
  - The potential difference between X and Y is greater than that between Y and W.
  - The potential difference between Y and Z is greater than that between Y and W.
  - The potential difference between X and Z is greater than that between Z and W.
  - The potential difference between X and W is greater than that across the battery.
  - The potential difference between X and Y is greater than that between Z and W.



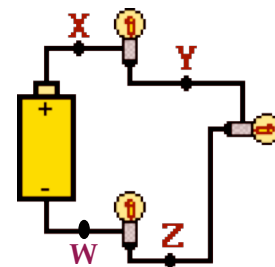12. Three identical light bulbs are connected to a battery as shown below. Which one of the following statements is true?
- All three bulbs will have the same brightness.
  - The bulb between X and Y will be the brightest.
  - The bulb between Y and Z will be the brightest.
  - The bulb between Z and the battery will be the brightest.

Justify your answer to this question using the language of physics.



13. Compare a circuit with three light bulbs to a circuit with two light bulbs. All light bulbs are identical. In which circuit will the overall power be the greatest? Intelligently defend your answer.